

# Henry's Bench



FINE MESH ...

\$14.97



BRIEFTON ...

\$29.97



LITTLE ...

\$219.99

Sections

## LED Current Control and The Arduino: Tutorial

Contents [hide]

- 1 Powering LEDs in Series
- 2 Where to Get the Parts
- 3 LM317 Voltage Regulator Pin Outs
- 4 The LM317 Voltage Regulator for Current Control
- 5 LM317 LED Current Control Test Circuit
- 6 Current Controlled LEDs with an Arduino Tutorial
  - 6.1 Build the Arduino Current Control LED Circuit
  - 6.2 Copy, Paste and Upload the Sketch
  - 6.3 Test the LED Current Control Project

### Powering LEDs in Series



Those of you who have used a [single 5mm LED with an Arduino](#) probably have used a currently limiting resistor in series the LED. Nothing wrong with that.



However another way to power the LED is to use current control. This has the advantage of allowing you to place multiple LEDs in series. This is because current control raises or lowers the voltage to control the current.

In this article, we will configure an LM317 to act as a current controller. This is not new stuff to those of us who have been chasing trons for a while, but is necessary if you wish to advance your Arduino expertise beyond the ability to use bricks.

Alas, this tutorial would not be complete without showing you how control these LEDs with your Arduino. Like some of my other tutorials, I will employ a TIP122 Darlington pair transistor to do just that.



Custom machine types. Get predictable costs and never overprovision again.



Google Cloud

TRY IT FREE

### Where to Get the Parts

In addition to your stash of resistors and LEDs, you will want the LM317 and TIP122.

The LM317 can be purchased at any of the retailers below:

[eBay](#)
[Amazon](#)
[Bangood](#)

The TIP122 can also be purchased from any of the following:

[eBay](#)
[Amazon](#)
[Deal Extreme](#)

### LM317 Voltage Regulator Pin Outs

The LM317 is most commonly found in a TO220 package. It only has three pins and we will be using all of them in this tutorial.

Select Language



Powered by Google Translate



LANGRIA EXECUTIVE ...

(1)

\$209.99

Shop now

AMAGABELI  
\$10.99KING KONG  
\$35.99


### Cell Phone & Arduino One Board!



What will you do with it?



[LANGRIA Executive Swivel Computer Gaming ...](#)

\$209.99

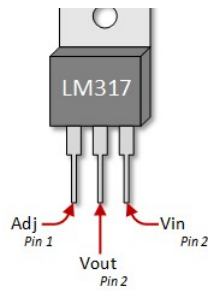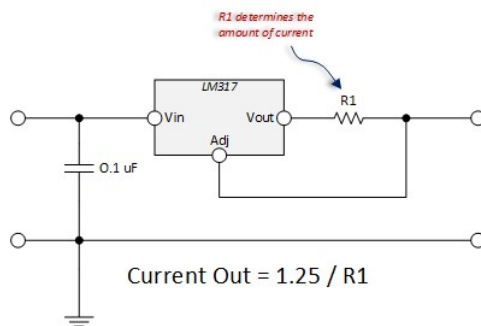

## The LM317 Voltage Regulator for Current Control

The use of an LM317 as a constant current source comes right from the data sheet. The schematic below shows how to configure the LM317 as a current regulator. It is the value of R1 that you will be concerned about and that value is determined by the type of LED you are using.



The math is really simple. The factor of 1.25 also comes from the data sheet.

Let's walk through an example:


1. Lets say you wanted to control to 300 mA. You would determine that your optimum resistor is:  
 **$R1 = 1.25 / 0.300 = 4.17 \text{ Ohms}$**
2. Next you're going to poke around in your box of resistors to see what you've got. You probably won't find that 4.17 Ohm resistor, so you will want to try something close. I had a 4.7 Ohm resistor.
3. Now you're going to want to apply the formula to see what that gets you.  
 **$\text{Current Out} = 1.25 / 4.7 = 266 \text{ mA}$**
4. Finally, we need to do a sanity check of the power rating of the resistor. Here we will use  $I^2 \times R$  to get the power dissipated by the resistor.  
 **$\text{Power Dissipated by Resistor} = 0.266^2 \times 4.7 = 0.332 \text{ Watts}$**  (a half watt resistor will do the trick)

If you're really particular about the current, you could search through that box of resistors to see what parallel resistor combination will get you to where you want to be. If you had a 47 ohm and a 4.7 ohm resistor, you would find that putting them in parallel would get you very close... like 4.16 Ohms. Take a look at this [Parallel Resistance Calculator](#).

## LM317 LED Current Control Test Circuit


For this tutorial, I'm using the super bright 3.5V, 1W LEDs. These LEDs happen to have a forward current of 350 mA. Since I've played with these for a bit, I happen to know that they will work just fine (albeit a little dimmer). If you want, put a 4.7 Ohm and a 15 Ohm Resistor in Parallel.

This is the circuit I have built.

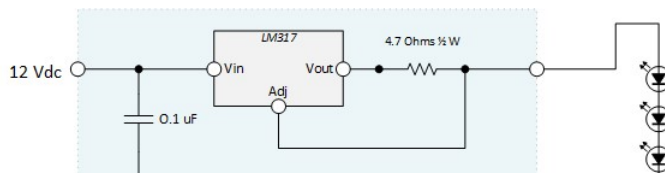

Shop Related Products



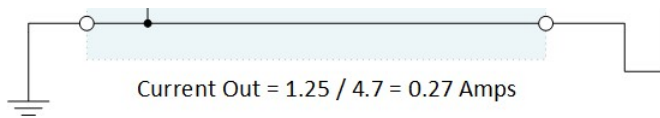

If you were to measure the voltage across each LED, you would find that they each drop about 3.2 Vdc for a total of 9.6 Vdc.


In truth, I set my adjustable supply to about 14V for this test. I did this because the LM317 wants an input voltage that is greater than 3 volts greater than the output.

If you were to reduce the number of LEDs to two, you find that the LM317 regulator sets the output across the LEDs to 6.4 Vdc to keep the current at the 266 mA set by the resistor.

## Current Controlled LEDs with an Arduino Tutorial
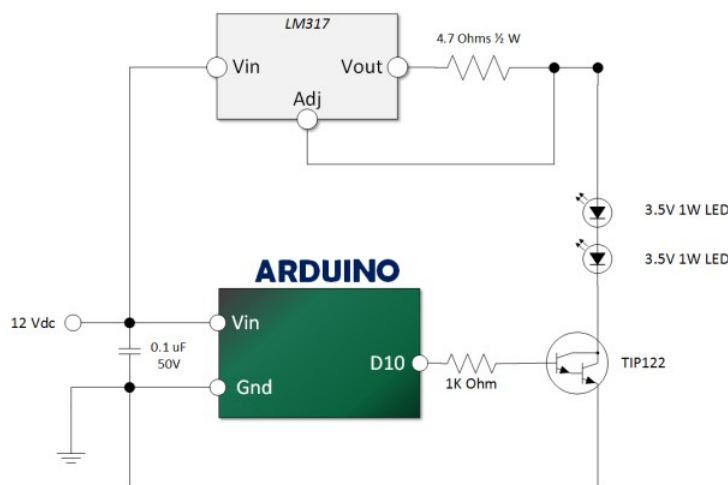
### Build the Arduino Current Control LED Circuit

We're going to use the TIP122 to sink the LEDs to ground. This transistor is more than capable of handling the 266 mA.



### Copy, Paste and Upload the Sketch

```
// Henry's Bench
//LED Current Control Tutorial Using an LM317

int nLedDrive = 10; // pin zero is our relay drive
int x; // Controls LED brightness

void setup() {
  pinMode(nLedDrive, OUTPUT); //
  digitalWrite(nLedDrive, HIGH); //Turn LED OFF
}

void loop() {

  for (x = 0; x < 256; x++){
    analogWrite(nLedDrive, x); // 0 is off, 255 is bright
    delay(10);
  }
}
```

### Test the LED Current Control Project

When you apply power, you will see the LEDs start dim and begin to brighten.

Aven 17010  
Adjustable Circu...

\$11.34

(815)

Cutequeen 750 pcs,30  
Values Resistor Kit x...

\$6.99

(69)



Major Brands LM317T  
Standard Regulator...

\$1.72

(50)



DROK Constant  
Current & Voltage...


\$34.99

(12)

Ads by Amazon




*3.3 & 5Vdc Supply*

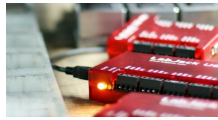

### LabJack, USB DAQ for \$115

Ad LabJack

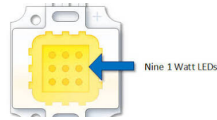

### 10 Watt High Power LED with an Arduino

capnfatz.com



### Square Air Core Inductors - Durable & Affordable

Ad uchida.cn




### Arduino Programmable Constant Current Power Supply

capnfatz.com




### ESP8266 Project Builder

Ad www.mydevices.com

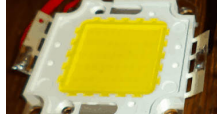


### How to Power a 50W Led with a Car Battery

capnfatz.com

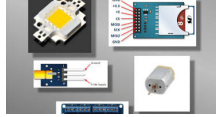

### Arduino Output Devices

capnfatz.com

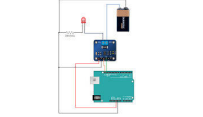

### INA219 Arduino Current Sensor Voltmeter Tutorial:...

capnfatz.com

Share this:

Share 2

Save 213

submit

Tweet

More

## 5 COMMENTS



July 28, 2017 J.Carlos

I liked the site and found it very good.

I'm making an adjustable source from 0V up to 30V with a 15 Amps output.

I would like to know how to connect a Transistor in the output, the LM 317 and LM 337 will only control the Transistor.

Someone knows how to do it or has a scheme.

Thank you friends

J.Carlos PU2OLT

<http://qslldobrasil.blogspot.com>

Sao Paulo-SP

Brazil



December 27, 2016 HAIKO

Thanks 🙌



November 24, 2016 Greg

I want to control the brightness of an LED using current control such as this. I don't want to use PWM due to potential interference patterns since it's being used as a back-light for camera sensor. Will using PWM on the TIP122 introduce a non-steady output on the LED or will it have a very stable output due to the voltage regulator?



May 27, 2016 capnfatz@gmail.com Author

Great question. I don't know. Would need a little more information.



May 26, 2016 · jeff

Great tutorial.

I'm wondering if I could use this as a starter to control the current to a coil so I can in turn control the magnetic field produced by the coil?

### ADD A COMMENT

*Your email address will not be published. Required fields are marked \**

Message\*

Name\*

Email\*

Website

Add Comment

---

Proudly powered by WordPress

RedWaves theme by Themient

↻