Arduino and AVR projects

Getting Extra Pins on ATtiny

4th June 2014

Part of the fun of designing with the ATtiny85 and ATtiny84 ranges is trying to shoehorn your project into the tiny package. I'm sure I'm not the first person who has run out of I/O pins while trying to use one for a project. Here are some tips I've discovered for making better use of the existing pins, or finding an extra pin.


Sharing inputs

How many inputs do you need to use to sense n pushbuttons?

The simplest method is to connect each pushbutton to a separate input. This requires n inputs.

For more than four pushbuttons it is better to arrange the pushbuttons into a x by y matrix, and multiplex them. This requires x+y inputs, so for 16 pushbuttons you need 8 inputs, or for n pushbuttons you need about root n inputs.

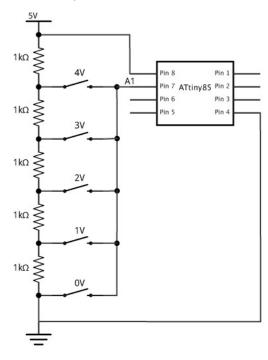A less obvious trick is to connect several pushbuttons to a single analogue input using a resistor ladder to give each button a different voltage. Here's an example with five buttons:



Connecting five pushbuttons to a single input.

The $1k\Omega$ resistors form a voltage divider, giving outputs of 0V, 1V, 2V, 3V, and 4V. With no button pressed the analogue input A0 is floating, so the internal pullup resistor should be enabled. Pressing a button sets A0 to the corresponding voltage.

To read which pushbutton is pressed we just need to do:

button = (analogRead(A0)*5+512)/1024;

which returns a number between 0 and 5.

The advantage of the above design is that it uses five identical resistors, so it's easy to construct. The disadvantage is that it draws current even when no button is pressed; in this case 1mA. Here's an alternative design that solves this problem:



Recent posts

▼ 2017

Four-Channel Thermometer Flexible GPS Parser Tiny Face Watch Driving Four RGB LEDs from an ATtiny85

Big Text for Little Display ATtiny85 Graphics Display Tiny Time 2 Watch

10 or 12-bit DAC from the ATtiny85

Simple 1-Wire Interface Audio Pitch Shifter Tiny Lisp Computer 2 PCB GameBone Simple Electronic

Game ▶ 2016

- ▶ 2015
- ▶ 2014

Topics

- ▶ Games
- ▶ Sound & Music
- ► Clocks
- ► GPS
- ► Tools
- ▶ Tutorials

By processor

- ► ATtiny85
- ► ATtiny84
- ► ATtiny841
- ► ATtiny2313
- ► ATtiny861
- ► ATmega328
- ► ATmega1284

About me

About me Contact me


Follow @technoblogy

Donate



Feeds

RSS feed

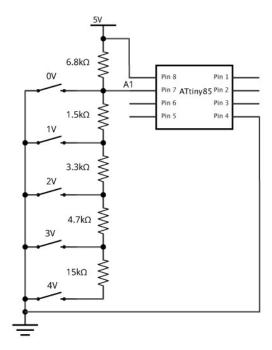


Connecting five pushbuttons to a single input.

Again, this gives voltages of 0V, 1V, 2V, 3V, and 4V, or 5V with no button pressed, but has the advantage that it draws no current when no button is pressed, and no pullup is needed. The resistors need to be in the ratios 12, 3, 5, 10, 30, but can be any suitably close values. I ran a program to find the best values from the E6 series; the values shown above produce voltages within 10% of the required values. Again, to read which pushbutton is pressed just do:

button = (analogRead(A0)*5+512)/1024;

Using a pin as both an input and an output

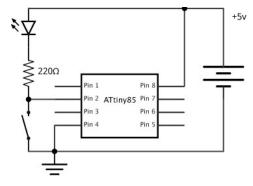Suppose you've got one pin available and you need to display status on an LED, and sense a pushbutton. One option is to use the same pin as both an input and an output:



Using a pin as both an input and an output.

Set the output low when you want to turn on the LED. Program it as an input when you want to turn off the LED, or read the pushbutton. You shouldn't set the output high since the pushbutton could then short the output to ground; to protect against this connect a second 220Ω resistor in series with the switch.

The only limitation is that the LED lights up while the pushbutton is pressed, but if the LED is showing the status of an option selected by the pushbutton that may actually be appropriate.

Here's a simple program that demonstrates this circuit; the LED is normally off, but pressing the pushbutton latches it on for one second:

int led = 3;

```
void setup() {
    digitalWrite(led, LOW);
    pinMode(led, INPUT);
}

void loop() {
    // Read input
    if (digitalRead(led) == LOW) {
        // Turn LED on
        pinMode(led, OUTPUT);
        delay(1000);
        // Turn LED off
        pinMode(led, INPUT);
    }
}
```

Using the reset pin on the ATtiny85

As is well known you can reprogram the internal fuses to reclaim the reset pin as an extra I/O pin. What is less well-known is that you can actually use the reset pin in a limited way on the ATtiny85 without having to reprogram the fuses, provide you avoid taking it below about 2.5V which will reset the chip.

Here's the program I used to test this on an ATtiny85 using the 1MHz internal clock:

```
/* Using the Reset pin as ADC0 */
const int Speaker = 3;
// Beep out a 10-bit binary number, LSB first
void debug (unsigned int thing) {
 for (unsigned int b=1; b!=1024; b = b<<1) {
    for (unsigned int i=0; i<1250; i++) {
     if (thing & b) digitalWrite(Speaker, (i & 16));
      else digitalWrite(Speaker, (i & 32));
   }
   for (unsigned int i=0; i<1250; i++) digitalWrite(Speaker, 0);
  }
}
void setup() {
 pinMode(Speaker, OUTPUT);
void loop() {
  debug(analogRead(0));
  delay(2000);
}
```


To reveal the ADC reading I've connected a piezo speaker between PB3 and ground, and I'm using a simple debug routine which beeps out the ten-bit ADC value as a series of low and high beeps, LSB first, with a low beep representing a 0 and a high beep representing a 1.

I tested it by connecting a potentiometer across the supply, with the wiper connected to the reset pin. Here are the results:

- 5v reading 0b11111111 or 1023
- 2.2V reading 0b0111000011 or 451
- Below 2.2V ATtiny85 reset

This corresponds to the datasheet, and gives us a range of 2.8V over which we can use the reset pin for analogue measurements.

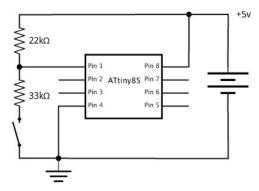
One simple application is to sense a pushbutton that switches ADC0 between 3v and 5v:



Using the reset pin on the ATtiny85.

Reprogramming the fuses to use the reset pin as an I/O pin

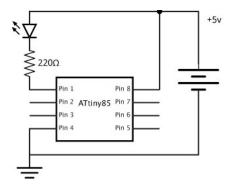If all else fails you can reprogram the fuses to use the reset pin as another I/O pin. This will enable you to use it as a digital or analogue input, or as an output to flash an LED:



Reprogramming the fuses to use the ATtiny85 reset pin as an I/O pin.

The problem is that once you have done that you will no longer be able to upload a program using an ISP programmer without first resetting the fuses using a high voltage programmer.

Here's the full procedure. First upload the program that will use the Reset pin. I'm using a simple Blink program to blink an LED, using the Reset pin as an output:

```
/* Blink Reset pin */
int led = 5; // Reset pin
void setup() {
   DDRB = 1<<led;
}
void loop() {
   PINB = 1<<led;
   delay(1000);
}</pre>
```

To program the ATtiny85 I used Sparkfun's Tiny AVR Programmer [1]. To use this with the Arduino IDE install the ATtiny microcontroller support for the Arduino IDE.

You now need to reprogram the High Fuses to 0x5f rather than 0xdf, to set the RSTDISBL fuse.

The simplest way is to use a high-voltage programmer, which lets you set the fuses to anything you want. You can use an Arduino Uno as a high-voltage programmer [2]. Alternatively Proto-Pic in the UK have produced a high-voltage programmer shield; all you need to do is supply is a 12V external power supply, plug in your ATtiny85, install the software, and program the device:



In the fuse reset program change the desired fuse configurations to:

```
// Desired fuse configuration
#define HFUSE 0x5F
#define LFUSE 0x62
```

and run the program to set the RSTDISBL fuse.

Now if you put the ATtiny85 back in the circuit the LED connected to pin 1, the reset pin, should flash as required. Note that the reset pin doesn't have such a high drive capability as the other pins, so the LED will be dimmer than an LED on pins 0 to 4.

Resetting the fuses to their defaults

If you've set the RSTDISBL fuse ISP programming will no longer work; next time you try to upload a program using the Tiny AVR Programmer you'll get the error:

avrdude: initialization failed, rc=-1

You will need to reset the fuses to their default values using the High-Voltage Programmer again before proceeding.

- 1. ^ Tiny AVR Programmer Hookup Guide on SparkFun.
- 2. ^ ATtiny Fuse Reset on Wayne's Tinkering Page.





jessey • 7 months ago

Hi, I hope someone here can help me. I tried to replicate your voltage divider at the top of this page that uses the $5-1~\rm K$ ohm resistors and am having a problem getting the code right on my attiny85, I'm sure the wiring is correct. I'm doing something wrong but just cant seem to figure out what I'm doing wrong. Here is the code I wrote to read three push buttons. Can someone have a look at my code and possibly advise me? I have 3 push buttons connected to 0V, 1V and 5V as the diagram above shows. I checked the voltage present on the analog pin for each of the 3 buttons and multiplied the voltage by 204.6 to get the numbers I'm using in the code, I found the math example

here -à

https://learn.sparkfun.com/... Only one of the push buttons work and that button is the code block at the bottom of the code.

Thanks

Copyright © 2014-2017 David Johnson-Davies